

1. What are the parameters of a dissipation-less line at radio frequencies?

- a) Resistance and capacitance
- b) Inductance and conductance
- c) Resistance and inductance
- d) Capacitance and conductance

Answer: b) Inductance and conductance

Explanation: A dissipation-less line at radio frequencies primarily exhibits inductance (L) and conductance (G), with negligible resistance and capacitance.

2. What are the characteristics of voltage and current on a dissipation-less line?

- a) Voltage and current are in phase
- b) Voltage leads current by 90 degrees
- c) Voltage lags current by 90 degrees
- d) Voltage and current are out of phase randomly

Answer: a) Voltage and current are in phase

Explanation: In a dissipation-less line, voltage and current are in phase with each other due to the absence of resistive losses.

3. What is the Standing Wave Ratio (SWR) a measure of?

- a) Efficiency of a transmission line
- b) Propagation speed of electromagnetic waves

- c) Mismatch in a transmission line
- d) Signal attenuation in a transmission line

Answer: c) Mismatch in a transmission line

Explanation: SWR measures the degree of mismatch between the transmission line and the load impedance.

4. What is the input impedance of an open circuit termination on a transmission line?

- a) Zero
- b) Infinity
- c) Depends on the frequency
- d) Depends on the length of the line

Answer: b) Infinity

Explanation: An open circuit termination results in an infinite input impedance due to the absence of a current path.

5. How is power measured on transmission lines?

- a) Directly by voltmeter and ammeter
- b) By calculating the product of voltage and current
- c) Through impedance matching
- d) By measuring the phase angle between voltage and current

Answer: b) By calculating the product of voltage and current

Explanation: Power on transmission lines is calculated by multiplying the voltage and current, typically using a wattmeter.

6. What type of transmission line is an eighth-wave line?

- a) Short-circuited line
- b) Open-circuited line
- c) Quarter-wave line
- d) Half-wave line

Answer: b) Open-circuited line

Explanation: An eighth-wave line is an open-circuited transmission line that is a multiple of one-eighth wavelength long.

7. What is the Smith chart used for in radio frequency engineering?

- a) Power measurement
- b) Impedance matching
- c) Wave propagation analysis
- d) Voltage measurement

Answer: b) Impedance matching

Explanation: The Smith chart is a graphical tool used for impedance matching and analyzing transmission line problems.

8. How can the Smith chart be utilized to solve transmission line problems?

- a) By directly measuring voltage and current
- b) By plotting impedance values and performing calculations
- c) By analyzing wave propagation speed
- d) By calculating standing wave ratios

Answer: b) By plotting impedance values and performing calculations

Explanation: The Smith chart allows engineers to plot complex impedance values and perform calculations to solve transmission line problems.

9. What is single stub matching used for in transmission lines?

- a) Impedance transformation
- b) Voltage measurement
- c) Power distribution
- d) Current measurement

Answer: a) Impedance transformation

Explanation: Single stub matching is a technique used to transform the impedance seen at one point along a transmission line to a desired value.

10. What is the purpose of double stub matching in radio frequency engineering?

- a) To increase power transmission efficiency
- b) To decrease standing wave ratio
- c) To achieve impedance matching
- d) To eliminate voltage fluctuations

Answer: c) To achieve impedance matching

Explanation: Double stub matching is a method used to achieve impedance matching in transmission lines by adjusting the positions and lengths of two stubs.

11. What is the primary characteristic of a quarter-wave line?

- a) Open circuit at one end
- b) Short circuit at one end
- c) Half the length of a half-wave line
- d) Double the length of an eighth-wave line

Answer: b) Short circuit at one end

Explanation: A quarter-wave line is characterized by a short circuit at one end and an open circuit at the other end.

12. In microstrip lines, where are the conductive traces usually located?

- a) Between two dielectric layers
- b) Embedded within a dielectric substrate
- c) Above a dielectric substrate
- d) Below a dielectric substrate

Answer: c) Above a dielectric substrate

Explanation: In microstrip lines, the conductive traces are typically located above a dielectric substrate.

13. What is the analysis method often used for microstrip lines?

- a) Transmission matrix analysis
- b) Finite element method
- c) Smith chart analysis
- d) Moment method

Answer: b) Finite element method

Explanation: The finite element method is commonly used for the analysis of microstrip lines due to its versatility and accuracy.

14. What does a half-wave line typically require at its termination points?

- a) Open circuit
- b) Short circuit
- c) Matching network
- d) Variable resistor

Answer: a) Open circuit

Explanation: A half-wave line typically requires an open circuit at its termination points for proper operation.

15. What property distinguishes a dissipation-less line from a typical transmission line?

- a) Higher power handling capacity
- b) Lower propagation speed

- c) Absence of resistive losses
- d) Higher standing wave ratio

Answer: c) Absence of resistive losses

Explanation: The primary distinction of a dissipation-less line is the absence of resistive losses, leading to theoretically infinite propagation of signals without attenuation.