

1.What is the basic building block of arithmetic circuits?

- A) Multiplexer
- B) Demultiplexer
- C) Adder
- D) Decoder

Answer: C) Adder

Explanation: Adder is the fundamental component used in arithmetic circuits for addition operations.

2.Which logic gate is used in the construction of a Half Adder?

- A) AND
- B) OR
- C) XOR
- D) NOT

Answer: C) XOR

Explanation: Half Adder consists of an XOR gate and an AND gate.

3.What is the function of a Full Adder?

- A) Adds two binary numbers
- B) Adds three binary numbers
- C) Adds two binary numbers with carry input
- D) Adds two decimal numbers

Answer: C) Adds two binary numbers with carry input

Explanation: Full Adder adds two binary numbers along with a carry input from the previous stage.

4.What is the difference between a Half Adder and a Full Adder?

- A) Half Adder has only one input
- B) Full Adder has an additional carry input
- C) Full Adder has only one output
- D) Half Adder has an additional carry input

Answer: B) Full Adder has an additional carry input

Explanation: Full Adder can add three inputs: two binary numbers and a carry input from the previous stage.

5.Which logic circuit is used to perform both addition and subtraction operations?

- A) Half Adder
- B) Half Subtractor
- C) Full Adder
- D) Full Subtractor

Answer: D) Full Subtractor

Explanation: Full Subtractor can perform both addition and subtraction.

6.What is the function of a Look-ahead carry generator?

- A) Generates carry-in bit
- B) Generates carry-out bit
- C) Generates carry-in and carry-out bits simultaneously
- D) Generates overflow flag

Answer: C) Generates carry-in and carry-out bits simultaneously

Explanation: Look-ahead carry generator predicts carry-out without waiting for the carry-in.

7.Which logic circuit is used to add Binary Coded Decimal (BCD) numbers?

- A) Half Adder
- B) Full Adder

- C) BCD Adder
- D) Full Subtractor

Answer: C) BCD Adder

Explanation: BCD Adder is designed specifically to add Binary Coded Decimal numbers.

8. In series addition of binary numbers, which bit is transmitted first?

- A) Least Significant Bit (LSB)
- B) Most Significant Bit (MSB)
- C) Carry bit
- D) Overflow bit

Answer: B) Most Significant Bit (MSB)

Explanation: In series addition, the MSB is transmitted first.

9. Which circuit is used to select one out of several input lines and route it to a single output line?

- A) Multiplexer
- B) Demultiplexer
- C) Encoder
- D) Decoder

Answer: A) Multiplexer

Explanation: Multiplexer selects one input line from multiple inputs and forwards it to a single output.

10. What is the function of a decoder?

- A) Converts binary data into its equivalent decimal form
- B) Converts decimal data into binary form
- C) Selects one output line from multiple input lines

D) Combines multiple input lines into a single output line

Answer: C) Selects one output line from multiple input lines

Explanation: Decoder decodes the input and selects one of the output lines based on the input code.

11. Which operation can an ALU (Arithmetic Logic Unit) not perform?

A) Addition

B) Subtraction

C) Multiplication

D) Division

Answer: D) Division

Explanation: ALU typically performs addition, subtraction, and logical operations but not division.

12. What does ALU stand for?

A) Arithmetic Logic Unit

B) Automated Logic Unit

C) Advanced Logic Unit

D) Algorithmic Logic Unit

Answer: A) Arithmetic Logic Unit

Explanation: ALU performs arithmetic and logical operations on data.

13. Which of the following is a parallel addition technique?

A) Ripple Carry Addition

B) Carry Look-ahead Addition

C) Series Addition

D) Both A and B

Answer: D) Both A and B

Explanation: Both Ripple Carry and Carry Look-ahead Addition are parallel addition techniques.

14. Which logic circuit is used to convert a binary number into its equivalent Gray code?

- A) Encoder
- B) Decoder
- C) Multiplexer
- D) Demultiplexer

Answer: A) Encoder

Explanation: Encoder converts binary data into a different format, such as Gray code.

15. What is the main advantage of parallel addition over serial addition?

- A) Lower hardware complexity
- B) Faster operation
- C) Reduced power consumption
- D) Easier implementation

Answer: B) Faster operation

Explanation: Parallel addition processes multiple bits simultaneously, resulting in faster operation.

16. Which logic circuit is used to combine multiple input lines into a single output line?

- A) Encoder
- B) Decoder
- C) Multiplexer
- D) Demultiplexer

Answer: C) Multiplexer

Explanation: Multiplexer selects one input line from multiple inputs and forwards it to a single output.

17. In a Full Subtractor, what inputs are required?

- A) Two binary numbers
- B) Two binary numbers and a borrow input
- C) Three binary numbers
- D) Three binary numbers and a borrow input

Answer: D) Three binary numbers and a borrow input

Explanation: Full Subtractor subtracts three binary numbers along with a borrow input from the previous stage.

18. Which logic circuit is used to divide one input into multiple outputs?

- A) Encoder
- B) Decoder
- C) Multiplexer
- D) Demultiplexer

Answer: D) Demultiplexer

Explanation: Demultiplexer divides a single input into multiple outputs.

19. What is the purpose of an encoder in digital electronics?

- A) To convert analog data to digital data
- B) To convert digital data to analog data
- C) To convert binary data to a more compact format
- D) To convert binary data to its equivalent Gray code

Answer: C) To convert binary data to a more compact format

Explanation: Encoder compresses binary data into a more compact format for transmission or

storage.

20. Which logic circuit is used to perform logical AND operation?

- A) Multiplexer
- B) Demultiplexer
- C) Encoder
- D) Gate

Answer: D) Gate

Explanation: Logic gates such as AND gate perform logical AND operations on input signals.

Related posts:

1. Introduction to Information Security
2. Introduction to Information Security MCQ
3. Introduction to Information Security MCQ
4. Symmetric Key Cryptography MCQ
5. Asymmetric Key Cryptography MCQ
6. Authentication & Integrity MCQ
7. E-mail, IP and Web Security MCQ