1. Which of the following is an advantage of digital instruments over analog instruments?

- a) Higher cost
- b) Limited accuracy
- c) Susceptible to noise
- d) Ease of interfacing with digital systems

Answer: d) Ease of interfacing with digital systems

Explanation: Digital instruments can easily communicate with other digital devices, making them suitable for integration into digital systems and automation.

2. What type of DAC uses a network of resistors to perform digital-to-analog conversion?

- a) Variable resistive type
- b) Binary ladder
- c) Weighted converter using Op-amp and transistor
- d) Dual Slope Integrating Type

Answer: a) Variable resistive type

Explanation: Variable resistive type DAC uses a network of resistors whose values can be varied to produce different analog output voltages corresponding to digital inputs.

3. Which DAC architecture employs a ladder network of resistors in a binary-weighted fashion?

a) R-2R ladder Type

- b) Binary ladder
- c) Weighted converter using Op-amp and transistor
- d) Ramp Technique

Answer: a) R-2R ladder Type

Explanation: R-2R ladder Type DAC utilizes a ladder network of resistors with a specific binary-weighted pattern to generate analog voltages.

4. In ADC, which technique involves charging a capacitor for a fixed period and measuring the voltage across it?

- a) Ramp Technique
- b) Integrating Type (voltage to frequency)
- c) Successive Approximations
- d) Dual Slope Integrating Type

Answer: d) Dual Slope Integrating Type

Explanation: In the Dual Slope Integrating Type ADC, a capacitor is charged for a fixed time interval, then discharged at a constant rate while measuring the voltage across it to determine the digital output.

5. What is the primary advantage of digital voltmeters compared to analog voltmeters?

- a) Higher sensitivity
- b) Lower resolution
- c) Susceptibility to environmental factors

d) Accuracy and precision

Answer: d) Accuracy and precision

Explanation: Digital voltmeters offer higher accuracy and precision compared to analog voltmeters, making them more reliable for precise measurements.

6. Which parameter determines the finest increment of measurement in a digital multimeter?

- a) Accuracy
- b) Sensitivity
- c) Resolution
- d) Precision

Answer: c) Resolution

Explanation: Resolution in a digital multi-meter refers to the smallest increment of measurement it can display, determining the level of detail in the measurements.

7. Which ADC technique involves comparing the input voltage with a known reference voltage and iteratively adjusting the digital output until the two voltages match?

- a) Ramp Technique
- b) Integrating Type (voltage to frequency)
- c) Successive Approximations
- d) Dual Slope Integrating Type

Answer: c) Successive Approximations

Explanation: Successive Approximations ADC compares the input voltage with a known reference voltage and iteratively refines the digital output to converge towards the input voltage.

8. Which DAC architecture utilizes the principle of weighted summing amplifiers to generate the analog output?

- a) R-2R ladder Type
- b) Binary ladder
- c) Weighted converter using Op-amp and transistor
- d) Practical DAC

Answer: c) Weighted converter using Op-amp and transistor

Explanation: Weighted converter using Op-amp and transistor DAC architecture utilizes weighted summing amplifiers to produce the analog output voltage.

9. What is the purpose of a ramp generator in the Ramp Technique ADC?

- a) To generate a reference voltage
- b) To produce a linearly increasing voltage
- c) To control the switching of analog switches
- d) To provide power to the Op-amp

Answer: b) To produce a linearly increasing voltage

Explanation: In the Ramp Technique ADC, the ramp generator generates a voltage that linearly increases with time, which is compared with the input voltage to determine the digital output.

10. Which type of DAC offers improved linearity and reduced complexity compared to other architectures?

- a) Binary ladder
- b) Weighted converter using Op-amp and transistor
- c) R-2R ladder Type
- d) Practical DAC

Answer: c) R-2R ladder Type

Explanation: R-2R ladder Type DAC provides improved linearity and reduced complexity compared to other DAC architectures, making it commonly used in many applications.

11. In ADC, which technique involves measuring the time taken for a voltage ramp to reach a certain level?

- a) Dual Slope Integrating Type
- b) Ramp Technique
- c) Integrating Type (voltage to frequency)
- d) Successive Approximations

Answer: a) Dual Slope Integrating Type

Explanation: In the Dual Slope Integrating Type ADC, the time taken for a voltage ramp to

reach a certain level is measured to determine the input voltage.

12. Which parameter of a digital multi-meter refers to its ability to detect small changes in input voltage?

- a) Accuracy
- b) Sensitivity
- c) Resolution
- d) Precision

Answer: b) Sensitivity

Explanation: Sensitivity in a digital multi-meter refers to its ability to detect small changes in input voltage, indicating its responsiveness to subtle variations.

13. What is the primary advantage of a practical DAC over other types?

- a) Higher cost
- b) Lower complexity
- c) Reduced linearity
- d) Limited resolution

Answer: b) Lower complexity

Explanation: Practical DACs offer lower complexity compared to other types, making them more straightforward to implement and integrate into systems.

14. Which ADC technique involves counting the number of clock pulses required for a ramp

signal to return to zero?

- a) Successive Approximations
- b) Ramp Technique
- c) Dual Slope Integrating Type
- d) Integrating Type (voltage to frequency)

Answer: c) Dual Slope Integrating Type

Explanation: In the Dual Slope Integrating Type ADC, the number of clock pulses required for a ramp signal to return to zero is counted to determine the input voltage.

15. What is the primary advantage of digital-to-analog conversion compared to analog-todigital conversion?

- a) Higher complexity
- b) Limited accuracy
- c) Ease of implementation
- d) Susceptibility to noise

Answer: c) Ease of implementation

Explanation: Digital-to-analog conversion is often easier to implement compared to analog-todigital conversion, especially in digital systems where processing and manipulation of digital signals are more straightforward.

Related posts:

- 1. Theory of Measurement MCQs
- 2. Cathode Ray Tubes, Oscilloscopes, and Bridge Circuits MCQs
- 3. Transducer MCQs
- 4. Signal and Function Generators, Displays MCQS
- 5. Web Development Essentials MCQs
- 6. HTML MCQs
- 7. Style sheets MCQs
- 8. XML MCQs
- 9. PHP and MySQL MCQs
- 10. Basics of programming MCQs
- 11. Decision control structure MCQs
- 12. Array MCQS
- 13. C Programming Essentials Structures, Preprocessor, and Unions MCQs
- 14. Basic concepts of OOP MCQS
- 15. Unix/Linux MCQs
- 16. The Shell Basic Commands, Shell Programming MCQs
- 17. File System MCQs
- 18. Process Control MCQS
- 19. System Security MCQs.
- 20. Dynamic Host Configuration Protocol MCQs
- 21. Introduction to Energy Science MCQs
- 22. Ecosystems mcqs
- 23. Biodiversity and its conservation MCQs
- 24. Environmental Pollution mcqs
- 25. Social Issues and the Environment mcqs

- 26. Signals and Systems MCQs
- 27. Linear Time- Invariant Systems mcqs
- 28. z-Transform mcqs
- 29. Fourier analysis of discrete time signals mcqs
- 30. State-Space Analysis, Sampling Theorem, and Signal Reconstruction mcqs
- 31. Frequency domain representation of signal mcqs
- 32. Modulation Techniques mcqs
- 33. FM Modulation & Transmission MCQs
- 34. Understanding AM and FM Transmission Noise and Receiver Characteristics
- 35. Control System MCQs: Basics, Feedback, and Analysis
- 36. Control System Analysis MCQs
- 37. Frequency Domain Analysis MCQs
- 38. System Design and Compensation Techniques MCQs
- 39. State Space & Control Systems MCQs
- 40. Feedback Amplifiers and Oscillators MCQs
- 41. Introduction to ICs and Op-Amps MCQs
- 42. Op-Amp Characteristics MCQs
- 43. OP-AMP applications MCQs
- 44. Electronic Circuits with 555 Timer MCQs
- 45. Voltage Regulator MCQs
- 46. Discrete-Time Signals and Systems MCqs
- 47. The z-Transformmcqs
- 48. Frequency Analysis of Discrete Time Signals mcqs
- 49. Efficient Computation of the DFT mcqs
- 50. Digital filters Design Techniques Mcqs
- 51. Radiation mcqs
- 52. Antenna Fundamentals mcqs

- 53. Types of antennas mcqs
- 54. Aperture and slot mcqs
- 55. Propagation of radio waves mcqs
- 56. Data Communication mcqs
- 57. OSI model mcqs
- 58. ERROR CONTROL AND DATA LINK PROTOCOLS mcqs
- 59. NETWORKS mcqs
- 60. NETWORKING DEVICES AND TCP / IP PROTOCOL SUITE mcqs
- 61. CMOS VLSI Circuit Design MCQs
- 62. Specification of sequential systems mcqs
- 63. Satellite Systems and Orbital Mechanics MCQs
- 64. Satellite Communication & Polarization MCQs
- 65. Satellite and Earth Segment MCQs
- 66. Satellite Communication MCQs
- 67. Satellite Services MCQs
- 68. 8051 Interfacing & Serial Communication MCQs
- 69. MCU Overview 8096 and PIC mcqs
- 70. Introduction to Embedded Systems mcqs
- 71. Embedded System Architecture mcqs
- 72. Input Output and Peripheral Devices mcqs
- 73. PHYSIOLOGY AND TRANSDUCERS mcqs
- 74. ELECTRO PHYSIOLOGICAL MEASUREMENTS mcqs
- 75. NON-ELECTRICAL PARAMETER MEASUREMENTS mcqs
- 76. MEDICAL IMAGING MCQS
- 77. ASSISTING AND THERAPEUTIC EQUIPMENTS MCQS
- 78. Power Semiconductor Switches MCQS
- 79. Rectifiers and Thyristors MCQs

- 80. Inverters & Cycloconverters Inverters MCQs
- 81. AC Voltage Controllers MCQs
- 82. DC DC Converters MCQS
- 83. Practical Consideration and Technology in VLSI Design MCQs
- 84. Device Modeling MCQs
- 85. Circuit Simulation MCQs
- 86. Structured Digital Circuits and Systems MCQs
- 87. CMOS Processing Technology MCQs
- 88. Microwave Engineering MCQs
- 89. Microwave Semiconductor Devices MCQs
- 90. RF Network Analysis & Measurement MCQs
- 91. Microwave Components and Circuits MCQs
- 92. RF & Microwave Circuit Design MCQs
- 93. Information Theory MCQs
- 94. Coding theorem MCQs
- 95. Information Channels MCQs
- 96. Error Control Coding MCQs
- 97. BCH and Convolutional Codes MCQs
- 98. Nanoscale Semiconductor Physics MCQs
- 99. Introduction to lithography MCQs
- 100. Tunnel Junctions and Tunneling Phenomena MCQs
- 101. Nanoelectronics MCQs
- 102. Scaling of physical systems MCQs
- 103. Cellular Mobile Systems MCQs
- 104. Wireless Communication Essentials MCQs
- 105. Cochannel interference reduction MCQs
- 106. Types of Noncochannel interference MCQS

- 107. Cellular Network Management MCQs
- 108. Digital Cellular Systems MCQs
- 109. IoT Essentials MCQs
- 110. IoT Technologies MCQs
- 111. Design Principles for Web Connectivity MCQs
- 112. IoT Technologies MCQS
- 113. IOT Design methodology MCQs
- 114. Probability and Random Variable MCQs
- 115. Probability Distributions and Expectations MCQs
- 116. Multiple Random Variables MCQS
- 117. Stochastic Processes MCQs
- 118. Optical Fiber Basics MCQs
- 119. Signal degradation in Optical Fibre MCQs
- 120. Optical sources and detectors MCQs
- 121. Optical Communication MCQs
- 122. Optical networks and amplifiers MCQS
- 123. 5G Wireless Communications MCQ
- 124. 5G Wireless Propagation Channels MCQS
- 125. 5G Transmission and Design Techniques MCQS
- 126. D2D and M2M Communications MCQS
- 127. Millimeter-Wave Communications MCQs
- 128. Review of Cellular Networks MCQS
- 129. LTE systems MCQS
- 130. Wireless Sensor Networks MCQS
- 131. Wireless routing Protocols MCQS
- 132. Internet of things (IoT) and GPS systems MCQS
- 133. Digital Image Processing MCQs

- 134. Transforms and Their Properties MCQs
- 135. Image Enhancement Techniques MCQs
- 136. Image Restoration MCQs
- 137. Compression & Image Watermarking MCQs
- 138. Speech Processing Fundamentals MCQs
- 139. Speech Distortion Analysis MCQs
- 140. HMMs in Speech Modeling MCQs
- 141. Large Vocabulary Continuous Speech RecognitioN MCQS
- 142. Text-to-Speech Synthesis MCQS
- 143. Number Systems MCQS
- 144. Combinational logic circuits MCQS
- 145. Sequential Logic Design MCQs
- 146. Registers and Counters MCQS
- 147. Logic Families and Semiconductor Memories MCQS
- 148. Semiconductor MCQs
- 149. Diode Circuits & Power Supply MCQs
- 150. Fundamentals of BJT MCQS
- 151. Small Signal analysis MCQs
- 152. Electronic Devices MCQs
- 153. Introduction to circuit theory MCQS
- 154. Network Graph theory MCQs
- 155. Network Theorems MCQS
- 156. Electrical Circuit Analysis and Laplace Transform MCQs
- 157. Two port parameters MCQS
- 158. Evolution of Microprocessors: From 8086 to Pentium MCQs
- 159. 8086 Microprocessor MCQs
- 160. Interfacing Chips in Microprocessor Systems MCQS

- 161. Peripheral Devices in Computer Systems MCQS
- 162. 8051 Microcontrollers & Embedded Systems MCQs
- 163. Sampling, Modulation, and Multiplexing MCQs
- 164. Digital Communication Techniques MCQs
- 165. Digital Modulation Techniques MCQs
- 166. Modulation Techniques and Signal Processing MCQs
- 167. Information Theory and Communication MCqs
- 168. Two-Port Networks and Matching Techniques MCQs
- 169. Passive LC Filters MCQs
- 170. Transmission Line Fundamentals MCQs
- 171. RF Transmission Lines and Matching Techniques: MCQs
- 172. Theodolite Traversing MCQs
- 173. Town Planning & Perspective Drawing MCQs
- 174. Dynamics of Flow MCQs
- 175. Preliminary and detailed investigation methods MCQs
- 176. Cost of Works MCQS
- 177. Urban Planning MCQs: Sustainability, Finance, and Emerging Concepts
- 178. Integrated Applications of Remote sensing and GIS MCQs
- 179. Small Business Setup MCQs
- 180. Virtual work and Energy Principles MCQS
- 181. Bridge Construction MCQs
- 182. Biological Treatment of waste-water MCQS
- 183. Multi Degree of Freedom System MCQS
- 184. Design of Beams MCQs
- 185. Wastewater Analysis & Disposal MCQs
- 186. Design Principles MCQs
- 187. Cost Effective & ECO-Friendly Structures MCQs

- 188. Forces on immersed bodies MCQs
- 189. Methods of Impact Identification MCQs
- 190. Decision Models MCQs
- 191. Groundwater and Well Dynamics MCQs
- 192. Types of Bridge Super Structures MCQs
- 193. Design of structure for earthquake resistance MCQS
- 194. Damage Assessment MCQs
- 195. Conventional and Non-conventional Techniques for Water Security MCQs
- 196. Harmonically excited Vibration MCQS
- 197. Dynamics of Engine Mechanisms MCQs
- 198. Automobile emissions MCQS
- 199. Quality Management process MCQs
- 200. Static & Dynamic Analysis MCQs