

1. What is the basic construction of a Bipolar Junction Transistor (BJT)?

- a) It consists of two layers of P-type semiconductor sandwiching a layer of N-type semiconductor
- b) It consists of two layers of N-type semiconductor sandwiching a layer of P-type semiconductor
- c) It consists of a single layer of semiconductor
- d) It consists of multiple layers of semiconductor stacked together

Answer: b) It consists of two layers of N-type semiconductor sandwiching a layer of P-type semiconductor

Explanation: A BJT typically consists of three semiconductor regions: emitter (N-type), base (P-type), and collector (N-type), forming a sandwich-like structure.

2. What is the primary current component in a Bipolar Junction Transistor (BJT)?

- a) Emitter current (I_E)
- b) Base current (I_B)
- c) Collector current (I_C)
- d) Leakage current

Answer: c) Collector current (I_C)

Explanation: Collector current (I_C) is the primary current component flowing through the collector terminal of a BJT.

3. Which configuration provides a high input impedance and low output impedance in a BJT

amplifier?

- a) Common Base (CB)
- b) Common Emitter (CE)
- c) Common Collector (CC)
- d) None of the above

Answer: a) Common Base (CB)

Explanation: Common Base configuration provides a high input impedance and low output impedance, making it suitable for impedance matching applications.

4. What effect causes the Early effect in Bipolar Junction Transistors (BJTs)?

- a) Base width modulation
- b) Avalanche breakdown
- c) Saturation current
- d) Thermal runaway

Answer: a) Base width modulation

Explanation: The Early effect, also known as base width modulation, causes an increase in the width of the base as the collector-base voltage increases, leading to a reduction in the effective base width and an increase in collector current.

5. In which region of operation does a BJT operate as an amplifier?

- a) Active region

- b) Cut-off region
- c) Saturation region
- d) Inverse region

Answer: a) Active region

Explanation: The active region is where a BJT operates as an amplifier, characterized by both junctions being forward-biased.

6. Which model is commonly used to describe the behavior of a BJT in terms of current components?

- a) Kirchhoff's laws
- b) Ohm's law
- c) Ebers-Moll model
- d) Maxwell's equations

Answer: c) Ebers-Moll model

Explanation: The Ebers-Moll model is commonly used to describe the behavior of a BJT in terms of its current components, considering both forward and reverse biased junctions.

7. What is the maximum power dissipation rating of a transistor denoted as?

- a) P_{max}
- b) P_d
- c) $V_{ce(max)}$
- d) $I_b(max)$

Answer: b) Pd

Explanation: The maximum power dissipation rating of a transistor is denoted as Pd, which represents the maximum amount of power the transistor can dissipate without being damaged.

8. Which biasing method provides the most stable operating point in a BJT amplifier circuit?

- a) Fixed bias
- b) Self bias
- c) Voltage Divider bias
- d) Collector to base bias

Answer: b) Self bias

Explanation: Self biasing provides automatic stabilization of the operating point, making it the most stable among the given biasing methods.

9. What is the purpose of load-line analysis in BJT amplifier circuits?

- a) To determine the gain of the amplifier
- b) To calculate the biasing resistors
- c) To establish the operating point
- d) To minimize power dissipation

Answer: c) To establish the operating point

Explanation: Load-line analysis is used to establish the operating point of a BJT amplifier

circuit by graphically determining the intersection of the load line with the DC load line.

10. In which biasing configuration is the base-emitter junction reverse-biased?

- a) Fixed bias
- b) Self bias
- c) Voltage Divider bias
- d) Collector to base bias

Answer: d) Collector to base bias

Explanation: In Collector to base bias configuration, the base-emitter junction is reverse-biased, providing stability to the operating point.

11. Which region of operation is characterized by both junctions of a BJT being reverse-biased?

- a) Active region
- b) Cut-off region
- c) Saturation region
- d) Inverse region

Answer: b) Cut-off region

Explanation: In the cut-off region, both the base-emitter and collector-base junctions of a BJT are reverse-biased, resulting in minimal collector current.

12. What type of transistor is sensitive to light and commonly used in optoelectronic

applications?

- a) NPN transistor
- b) PNP transistor
- c) JFET
- d) Phototransistor

Answer: d) Phototransistor

Explanation: Phototransistors are transistors that are sensitive to light and are commonly used in optoelectronic applications for light detection and sensing.

13. Which method of bias stabilization uses a resistor connected between the collector and base terminals?

- a) Fixed bias
- b) Self bias
- c) Voltage Divider bias
- d) Collector to base bias

Answer: d) Collector to base bias

Explanation: Collector to base bias stabilization method uses a resistor connected between the collector and base terminals to stabilize the operating point.

14. What is the main purpose of transistor biasing circuits?

- a) To control the transistor's switching speed

- b) To control the transistor's amplification factor
- c) To establish the operating point
- d) To minimize power dissipation

Answer: c) To establish the operating point

Explanation: Transistor biasing circuits are used to establish the operating point of the transistor, ensuring proper amplification or switching behavior.

15. What happens to the collector current in a BJT when it operates in the saturation region?

- a) It decreases
- b) It remains constant
- c) It increases
- d) It becomes zero

Answer: c) It increases

Explanation: In the saturation region, the collector current of a BJT increases significantly due to both junctions being forward-biased and allowing maximum current flow.

16. Which configuration of a BJT amplifier provides a voltage gain greater than unity?

- a) Common Base (CB)
- b) Common Emitter (CE)
- c) Common Collector (CC)
- d) None of the above

Answer: b) Common Emitter (CE)

Explanation: Common Emitter configuration provides a voltage gain greater than unity, making it suitable for voltage amplification applications.

17. What effect can cause a BJT to undergo thermal runaway?

- a) Base width modulation
- b) Avalanche breakdown
- c) Saturation current
- d) Excessive heating

Answer: d) Excessive heating

Explanation: Excessive heating can cause a BJT to undergo thermal runaway, where increasing temperature leads to increased collector current, further heating the device.

18. What is the primary purpose of a BJT used as a switch?

- a) To amplify signals
- b) To regulate voltage
- c) To control current flow
- d) To generate oscillations

Answer: c) To control current flow

Explanation: A BJT used as a switch is primarily employed to control the flow of current through a circuit, either allowing it to flow (ON state) or preventing it (OFF state).

19. What is the primary difference between CB, CE, and CC configurations in a BJT amplifier?

- a) Their voltage gains
- b) Their input and output impedance
- c) Their biasing methods
- d) Their current gains

Answer: b) Their input and output impedance

Explanation: The primary difference between CB, CE, and CC configurations lies in their input and output impedance characteristics, affecting their suitability for different applications.

20. Which of the following is NOT a biasing method for BJT transistors?

- a) Fixed bias
- b) Thermal bias
- c) Voltage Divider bias
- d) Collector to base bias

Answer: b) Thermal bias

Explanation: "Thermal bias" is not a commonly recognized biasing method for BJT transistors. The other options are all valid methods used in transistor biasing circuits.

Related posts:

1. Semiconductor MCQs
2. Diode Circuits & Power Supply MCQs

3. Small Signal analysis MCQs
4. Electronic Devices MCQs
5. Web Development Essentials MCQs
6. HTML MCQs
7. Style sheets MCQs
8. XML MCQs
9. PHP and MySQL MCQs
10. Basics of programming MCQs
11. Decision control structure MCQs
12. Array MCQS
13. C Programming Essentials Structures, Preprocessor, and Unions MCQs
14. Basic concepts of OOP MCQS
15. Unix/Linux MCQs
16. The Shell Basic Commands, Shell Programming MCQs
17. File System MCQs
18. Process Control MCQS
19. System Security MCQs.
20. Dynamic Host Configuration Protocol MCQs
21. Introduction to Energy Science MCQs
22. Ecosystems mcqs
23. Biodiversity and its conservation MCQs
24. Environmental Pollution mcqs
25. Social Issues and the Environment mcqs
26. Signals and Systems MCQs
27. Linear Time- Invariant Systems mcqs
28. z-Transform mcqs
29. Fourier analysis of discrete time signals mcqs

30. State-Space Analysis, Sampling Theorem, and Signal Reconstruction mcqs
31. Frequency domain representation of signal mcqs
32. Modulation Techniques mcqs
33. FM Modulation & Transmission MCQs
34. Understanding AM and FM Transmission Noise and Receiver Characteristics
35. Control System MCQs: Basics, Feedback, and Analysis
36. Control System Analysis MCQs
37. Frequency Domain Analysis MCQs
38. System Design and Compensation Techniques MCQs
39. State Space & Control Systems MCQs
40. Feedback Amplifiers and Oscillators MCQs
41. Introduction to ICs and Op-Amps MCQs
42. Op-Amp Characteristics MCQs
43. OP-AMP applications MCQs
44. Electronic Circuits with 555 Timer MCQs
45. Voltage Regulator MCQs
46. Discrete-Time Signals and Systems MCqs
47. The z-Transformmcqs
48. Frequency Analysis of Discrete Time Signals mcqs
49. Efficient Computation of the DFT mcqs
50. Digital filters Design Techniques Mcqs
51. Radiation mcqs
52. Antenna Fundamentals mcqs
53. Types of antennas mcqs
54. Aperture and slot mcqs
55. Propagation of radio waves mcqs
56. Data Communication mcqs

57. OSI model mcqs
58. ERROR CONTROL AND DATA LINK PROTOCOLS mcqs
59. NETWORKS mcqs
60. NETWORKING DEVICES AND TCP / IP PROTOCOL SUITE mcqs
61. CMOS VLSI Circuit Design MCQs
62. Specification of sequential systems mcqs
63. Satellite Systems and Orbital Mechanics MCQs
64. Satellite Communication & Polarization MCQs
65. Satellite and Earth Segment MCQs
66. Satellite Communication MCQs
67. Satellite Services MCQs
68. 8051 Interfacing & Serial Communication MCQs
69. MCU Overview 8096 and PIC mcqs
70. Introduction to Embedded Systems mcqs
71. Embedded System Architecture mcqs
72. Input Output and Peripheral Devices mcqs
73. PHYSIOLOGY AND TRANSDUCERS mcqs
74. ELECTRO - PHYSIOLOGICAL MEASUREMENTS mcqs
75. NON-ELECTRICAL PARAMETER MEASUREMENTS mcqs
76. MEDICAL IMAGING MCQS
77. ASSISTING AND THERAPEUTIC EQUIPMENTS MCQS
78. Power Semiconductor Switches MCQS
79. Rectifiers and Thyristors MCQs
80. Inverters & Cycloconverters Inverters MCQs
81. AC Voltage Controllers MCQs
82. DC - DC Converters MCQS
83. Practical Consideration and Technology in VLSI Design MCQs

84. Device Modeling MCQs
85. Circuit Simulation MCQs
86. Structured Digital Circuits and Systems MCQs
87. CMOS Processing Technology MCQs
88. Microwave Engineering MCQs
89. Microwave Semiconductor Devices MCQs
90. RF Network Analysis & Measurement MCQs
91. Microwave Components and Circuits MCQs
92. RF & Microwave Circuit Design MCQs
93. Information Theory MCQs
94. Coding theorem MCQs
95. Information Channels MCQs
96. Error Control Coding MCQs
97. BCH and Convolutional Codes MCQs
98. Nanoscale Semiconductor Physics MCQs
99. Introduction to lithography MCQs
100. Tunnel Junctions and Tunneling Phenomena MCQs
101. Nanoelectronics MCQs
102. Scaling of physical systems MCQs
103. Cellular Mobile Systems MCQs
104. Wireless Communication Essentials MCQs
105. Cochannel interference reduction MCQs
106. Types of Noncochannel interference MCQS
107. Cellular Network Management MCQs
108. Digital Cellular Systems MCQs
109. IoT Essentials MCQs
110. IoT Technologies MCQs

111. Design Principles for Web Connectivity MCQs
112. IoT Technologies MCQS
113. IOT Design methodology MCQs
114. Probability and Random Variable MCQs
115. Probability Distributions and Expectations MCQs
116. Multiple Random Variables MCQS
117. Stochastic Processes MCQs
118. Optical Fiber Basics MCQs
119. Signal degradation in Optical Fibre MCQs
120. Optical sources and detectors MCQs
121. Optical Communication MCQs
122. Optical networks and amplifiers MCQS
123. 5G Wireless Communications MCQ
124. 5G Wireless Propagation Channels MCQS
125. 5G Transmission and Design Techniques MCQS
126. D2D and M2M Communications MCQS
127. Millimeter-Wave Communications MCQs
128. Review of Cellular Networks MCQS
129. LTE systems MCQS
130. Wireless Sensor Networks MCQS
131. Wireless routing Protocols MCQS
132. Internet of things (IoT) and GPS systems MCQS
133. Digital Image Processing MCQs
134. Transforms and Their Properties MCQs
135. Image Enhancement Techniques MCQs
136. Image Restoration MCQs
137. Compression & Image Watermarking MCQs

138. Speech Processing Fundamentals MCQs
139. Speech Distortion Analysis MCQs
140. HMMs in Speech Modeling MCQs
141. Large Vocabulary Continuous Speech Recognition MCQS
142. Text-to-Speech Synthesis MCQS
143. Theory of Measurement MCQs
144. Cathode Ray Tubes, Oscilloscopes, and Bridge Circuits MCQs
145. Transducer MCQs
146. Signal and Function Generators, Displays MCQS
147. Digital and Analog Conversion MCQs
148. Number Systems MCQS
149. Combinational logic circuits MCQS
150. Sequential Logic Design MCQs
151. Registers and Counters MCQS
152. Logic Families and Semiconductor Memories MCQS
153. Introduction to circuit theory MCQS
154. Network Graph theory MCQs
155. Network Theorems MCQS
156. Electrical Circuit Analysis and Laplace Transform MCQs
157. Two port parameters MCQS
158. Evolution of Microprocessors: From 8086 to Pentium MCQs
159. 8086 Microprocessor MCQs
160. Interfacing Chips in Microprocessor Systems MCQS
161. Peripheral Devices in Computer Systems MCQS
162. 8051 Microcontrollers & Embedded Systems MCQs
163. Sampling, Modulation, and Multiplexing MCQs
164. Digital Communication Techniques MCQs

165. Digital Modulation Techniques MCQs
166. Modulation Techniques and Signal Processing MCQs
167. Information Theory and Communication MCqs
168. Two-Port Networks and Matching Techniques MCQs
169. Passive LC Filters MCQs
170. Transmission Line Fundamentals MCQs
171. RF Transmission Lines and Matching Techniques: MCQs
172. Block Chain MCQs
173. Machine Learning MCQs
174. Programming Practices MCQ
175. Ecosystems MCQ
176. Biodiversity and its conservation MCQ
177. Graph Theory and Combinatorics MCQ
178. Relational algebra, Functions and graph theory MCQ
179. Combinational Logic MCQ
180. Sequential logic MCQ
181. Polymorphism MCQ
182. Library Management System MCQ
183. Algorithmic Problem MCQ
184. Trees, Graphs, and NP-Completeness MCQ
185. Computer Arithmetic MCQ
186. I/O Organization MCQ
187. Input / Output MCQ
188. Operating Systems and Concurrency
189. Fuzzy Systems MCQ
190. Genetic Algorithms MCQ
191. RL Techniques MCQs

- 192. Review of traditional networks MCQ
- 193. NoSQL MCQs Concepts, Variations, and MongoDB
- 194. Mining social Network Graphs MCQ
- 195. OLAP Systems MCQ
- 196. Introduction to Data& Data Mining MCQ
- 197. Agile Software Design and Development MCQs
- 198. Machine Learning Fundamentals MCQs
- 199. MAC Sub layer MCQ
- 200. Network Layer MCQ