

1. Which configuration of an operational amplifier (op-amp) provides a phase shift of 180 degrees between input and output?

- a) Inverting amplifier
- b) Non-inverting amplifier
- c) Summing amplifier
- d) Integrator

Answer: a) Inverting amplifier

Explanation: In an inverting amplifier configuration, the output signal is 180 degrees out of phase with the input signal.

2. What is the primary function of a differential input and differential output amplifier?

- a) Increase signal gain
- b) Provide isolation between input and output
- c) Amplify the difference between two input voltages
- d) Generate a sinusoidal output

Answer: c) Amplify the difference between two input voltages

Explanation: Differential amplifiers amplify the voltage difference between two input terminals.

3. Which type of feedback is employed in a voltage-series feedback amplifier?

- a) Positive feedback
- b) Negative feedback
- c) No feedback
- d) Voltage divider feedback

Answer: b) Negative feedback

Explanation: Voltage-series feedback amplifier uses negative feedback to stabilize gain and performance.

4. What is the function of a log/antilog amplifier?

- a) Amplify high-frequency signals
- b) Perform logarithmic or antilogarithmic operations on input signals
- c) Generate triangular waveforms
- d) Act as a voltage-controlled oscillator

Answer: b) Perform logarithmic or antilogarithmic operations on input signals

Explanation: Log/antilog amplifiers are used to convert signals into logarithmic or antilogarithmic scales.

5. Which type of filter exhibits a constant gain within its passband and a sharp roll-off beyond the cutoff frequency?

- a) Butterworth filter
- b) Chebyshev filter
- c) Band reject filter
- d) Notch filter

Answer: a) Butterworth filter

Explanation: Butterworth filters have a maximally flat magnitude response in the passband.

6. What is the characteristic of a high pass filter?

- a) Passes low-frequency signals
- b) Attenuates low-frequency signals
- c) Passes high-frequency signals
- d) Attenuates high-frequency signals

Answer: c) Passes high-frequency signals

Explanation: High pass filters allow high-frequency signals to pass through while attenuating low-frequency signals.

7. Which type of filter is designed to attenuate a specific range of frequencies while allowing all others to pass?

- a) Low pass filter
- b) High pass filter
- c) Band pass filter
- d) Band reject filter

Answer: d) Band reject filter

Explanation: Band reject filters attenuate a specific range of frequencies while allowing all others to pass.

8. What is the primary purpose of an analog multiplier such as MPY634?

- a) Generate sine waves
- b) Perform mathematical operations on analog signals
- c) Convert digital signals to analog
- d) Amplify audio signals

Answer: b) Perform mathematical operations on analog signals

Explanation: Analog multipliers are used to perform mathematical operations like multiplication on analog signals.

9. Which type of oscillator generates triangular or rectangular waveforms?

- a) Phase-shift oscillator
- b) Wein bridge oscillator
- c) Triangular wave oscillator
- d) Rectangular wave oscillator

Answer: c) Triangular wave oscillator

Explanation: Triangular wave oscillators generate triangular waveforms.

10. What is the primary function of a comparator?

- a) Amplify input signals
- b) Provide linear output
- c) Compare two input voltages and produce a digital output
- d) Generate sinusoidal waveforms

Answer: c) Compare two input voltages and produce a digital output

Explanation: Comparators compare two input voltages and produce a digital output based on their relative magnitudes.

11. What is the primary application of a zero-crossing detector?

- a) Generating square wave signals
- b) Detecting the zero points of a waveform
- c) Filtering out low-frequency noise
- d) Amplifying high-frequency signals

Answer: b) Detecting the zero points of a waveform

Explanation: Zero-crossing detectors detect the points at which a waveform crosses the zero axis.

12. How does an integrator differ from a differentiator in terms of their output response to input signals?

- a) Integrator outputs a derivative, while differentiator outputs an integral
- b) Integrator outputs an integral, while differentiator outputs a derivative
- c) Both integrator and differentiator output the same response
- d) Integrator amplifies, while differentiator attenuates input signals

Answer: b) Integrator outputs an integral, while differentiator outputs a derivative

Explanation: Integrators produce an output signal that is the integral of the input signal, while differentiators produce an output signal that is the derivative of the input signal.

13. What is the primary function of AGC (Automatic Gain Control) in op-amp circuits?

- a) Provide constant voltage supply
- b) Adjust the gain of the amplifier to maintain a constant output level
- c) Generate sinusoidal waveforms
- d) Stabilize the operating temperature

Answer: b) Adjust the gain of the amplifier to maintain a constant output level

Explanation: AGC adjusts the gain of the amplifier to maintain a constant output level despite changes in input signal strength.

14. Which type of filter is designed to pass a specific range of frequencies while attenuating all others?

- a) Band reject filter
- b) Low pass filter
- c) High pass filter
- d) Band pass filter

Answer: d) Band pass filter

Explanation: Band pass filters allow a specific range of frequencies to pass through while attenuating frequencies outside that range.

15. What is the primary application of an instrumentation amplifier?

- a) Audio amplification
- b) Measuring small differential voltages accurately
- c) Generating square wave signals
- d) Filtering out high-frequency noise

Answer: b) Measuring small differential voltages accurately

Explanation: Instrumentation amplifiers are used for precise measurement of small differential voltages, often in sensor applications.

16. What is the purpose of a phase-shift oscillator?

- a) To shift the phase of input signals by 180 degrees
- b) To generate sinusoidal output signals
- c) To amplify input signals
- d) To compare two input signals

Answer: b) To generate sinusoidal output signals

Explanation: Phase-shift oscillators generate sinusoidal output signals.

17. Which type of feedback is employed in a voltage-shunt feedback amplifier?

- a) Positive feedback
- b) Negative feedback
- c) No feedback
- d) Voltage divider feedback

Answer: b) Negative feedback

Explanation: Voltage-shunt feedback amplifier uses negative feedback to stabilize gain and performance.

18. What is the primary function of a summing amplifier?

- a) Amplify the sum of multiple input signals
- b) Provide isolation between input and output
- c) Generate square wave signals
- d) Filter out high-frequency noise

Answer: a) Amplify the sum of multiple input signals

Explanation: Summing amplifiers add together multiple input signals with weighted coefficients.

19. What is the main difference between a Wein bridge oscillator and a phase-shift oscillator?

- a) Wein bridge oscillator produces square wave outputs, while phase-shift oscillator produces sinusoidal outputs
- b) Wein bridge oscillator uses RC feedback network, while phase-shift oscillator uses an inverting amplifier
- c) Wein bridge oscillator provides frequency stability, while phase-shift oscillator provides amplitude stability
- d) Wein bridge oscillator employs an operational amplifier, while phase-shift oscillator does not

Answer: c) Wein bridge oscillator provides frequency stability, while phase-shift oscillator provides amplitude stability

Explanation: Wein bridge oscillators are known for their frequency stability, while phase-shift oscillators are known for their amplitude stability.

20. Which type of filter is commonly used in audio applications to separate bass frequencies from midrange and treble frequencies?

- a) Low pass filter
- b) High pass filter

- c) Band pass filter
- d) Band reject filter

Answer: a) Low pass filter

Explanation: Low pass filters allow low-frequency signals, such as bass, to pass through while attenuating higher frequencies.

Related Posts:

1. Feedback Amplifiers and Oscillators MCQs
2. Introduction to ICs and Op-Amps MCQs
3. Op-Amp Characteristics MCQs
4. Electronic Circuits with 555 Timer MCQs
5. Voltage Regulator MCQs
6. Web Development Essentials MCQs
7. HTML MCQs
8. Style sheets MCQs
9. XML MCQs
10. PHP and MySQL MCQs
11. Basics of programming MCQs
12. Decision control structure MCQs
13. Array MCQS
14. C Programming Essentials Structures, Preprocessor, and Unions MCQs
15. Basic concepts of OOP MCQS
16. Unix/Linux MCQs
17. The Shell Basic Commands, Shell Programming MCQs
18. File System MCQs
19. Process Control MCQS

20. System Security MCQs.
21. Dynamic Host Configuration Protocol MCQs
22. Introduction to Energy Science MCQs
23. Ecosystems mcqs
24. Biodiversity and its conservation MCQs
25. Environmental Pollution mcqs
26. Social Issues and the Environment mcqs
27. Signals and Systems MCQs
28. Linear Time- Invariant Systems mcqs
29. z-Transform mcqs
30. Fourier analysis of discrete time signals mcqs
31. State-Space Analysis, Sampling Theorem, and Signal Reconstruction mcqs
32. Frequency domain representation of signal mcqs
33. Modulation Techniques mcqs
34. FM Modulation & Transmission MCQs
35. Understanding AM and FM Transmission Noise and Receiver Characteristics
36. Control System MCQs: Basics, Feedback, and Analysis
37. Control System Analysis MCQs
38. Frequency Domain Analysis MCQs
39. System Design and Compensation Techniques MCQs
40. State Space & Control Systems MCQs
41. Discrete-Time Signals and Systems MCqs
42. The z-Transformmcqs
43. Frequency Analysis of Discrete Time Signals mcqs
44. Efficient Computation of the DFT mcqs
45. Digital filters Design Techniques Mcqs
46. Radiation mcqs

47. Antenna Fundamentals mcqs
48. Types of antennas mcqs
49. Aperture and slot mcqs
50. Propagation of radio waves mcqs
51. Data Communication mcqs
52. OSI model mcqs
53. ERROR CONTROL AND DATA LINK PROTOCOLS mcqs
54. NETWORKS mcqs
55. NETWORKING DEVICES AND TCP / IP PROTOCOL SUITE mcqs
56. CMOS VLSI Circuit Design MCQs
57. Specification of sequential systems mcqs
58. Satellite Systems and Orbital Mechanics MCQs
59. Satellite Communication & Polarization MCQs
60. Satellite and Earth Segment MCQs
61. Satellite Communication MCQs
62. Satellite Services MCQs
63. 8051 Interfacing & Serial Communication MCQs
64. MCU Overview 8096 and PIC mcqs
65. Introduction to Embedded Systems mcqs
66. Embedded System Architecture mcqs
67. Input Output and Peripheral Devices mcqs
68. PHYSIOLOGY AND TRANSDUCERS mcqs
69. ELECTRO - PHYSIOLOGICAL MEASUREMENTS mcqs
70. NON-ELECTRICAL PARAMETER MEASUREMENTS mcqs
71. MEDICAL IMAGING MCQS
72. ASSISTING AND THERAPEUTIC EQUIPMENTS MCQS
73. Power Semiconductor Switches MCQS

74. Rectifiers and Thyristors MCQs
75. Inverters & Cycloconverters Inverters MCQs
76. AC Voltage Controllers MCQs
77. DC – DC Converters MCQS
78. Practical Consideration and Technology in VLSI Design MCQs
79. Device Modeling MCQs
80. Circuit Simulation MCQs
81. Structured Digital Circuits and Systems MCQs
82. CMOS Processing Technology MCQs
83. Microwave Engineering MCQs
84. Microwave Semiconductor Devices MCQs
85. RF Network Analysis & Measurement MCQs
86. Microwave Components and Circuits MCQs
87. RF & Microwave Circuit Design MCQs
88. Information Theory MCQs
89. Coding theorem MCQs
90. Information Channels MCQs
91. Error Control Coding MCQs
92. BCH and Convolutional Codes MCQs
93. Nanoscale Semiconductor Physics MCQs
94. Introduction to lithography MCQs
95. Tunnel Junctions and Tunneling Phenomena MCQs
96. Nanoelectronics MCQs
97. Scaling of physical systems MCQs
98. Cellular Mobile Systems MCQs
99. Wireless Communication Essentials MCQs
100. Cochannel interference reduction MCQs

101. Types of Noncochannel interference MCQS
102. Cellular Network Management MCQs
103. Digital Cellular Systems MCQs
104. IoT Essentials MCQs
105. IoT Technologies MCQs
106. Design Principles for Web Connectivity MCQs
107. IoT Technologies MCQS
108. IOT Design methodology MCQs
109. Probability and Random Variable MCQs
110. Probability Distributions and Expectations MCQs
111. Multiple Random Variables MCQS
112. Stochastic Processes MCQs
113. Optical Fiber Basics MCQs
114. Signal degradation in Optical Fibre MCQs
115. Optical sources and detectors MCQs
116. Optical Communication MCQs
117. Optical networks and amplifiers MCQS
118. 5G Wireless Communications MCQ
119. 5G Wireless Propagation Channels MCQS
120. 5G Transmission and Design Techniques MCQS
121. D2D and M2M Communications MCQS
122. Millimeter-Wave Communications MCQs
123. Review of Cellular Networks MCQS
124. LTE systems MCQS
125. Wireless Sensor Networks MCQS
126. Wireless routing Protocols MCQS
127. Internet of things (IoT) and GPS systems MCQS

- 128. Digital Image Processing MCQs
- 129. Transforms and Their Properties MCQs
- 130. Image Enhancement Techniques MCQs
- 131. Image Restoration MCQs
- 132. Compression & Image Watermarking MCQs
- 133. Speech Processing Fundamentals MCQs
- 134. Speech Distortion Analysis MCQs
- 135. HMMs in Speech Modeling MCQs
- 136. Large Vocabulary Continuous Speech Recognition MCQS
- 137. Text-to-Speech Synthesis MCQS
- 138. Theory of Measurement MCQs
- 139. Cathode Ray Tubes, Oscilloscopes, and Bridge Circuits MCQs
- 140. Transducer MCQs
- 141. Signal and Function Generators, Displays MCQS
- 142. Digital and Analog Conversion MCQs
- 143. Number Systems MCQS
- 144. Combinational logic circuits MCQS
- 145. Sequential Logic Design MCQs
- 146. Registers and Counters MCQS
- 147. Logic Families and Semiconductor Memories MCQS
- 148. Semiconductor MCQs
- 149. Diode Circuits & Power Supply MCQs
- 150. Fundamentals of BJT MCQS
- 151. Small Signal analysis MCQs
- 152. Electronic Devices MCQs
- 153. Introduction to circuit theory MCQS
- 154. Network Graph theory MCQs

- 155. Network Theorems MCQS
- 156. Electrical Circuit Analysis and Laplace Transform MCQs
- 157. Two port parameters MCQS
- 158. Evolution of Microprocessors: From 8086 to Pentium MCQs
- 159. 8086 Microprocessor MCQs
- 160. Interfacing Chips in Microprocessor Systems MCQS
- 161. Peripheral Devices in Computer Systems MCQS
- 162. 8051 Microcontrollers & Embedded Systems MCQs
- 163. Sampling, Modulation, and Multiplexing MCQs
- 164. Digital Communication Techniques MCQs
- 165. Digital Modulation Techniques MCQs
- 166. Modulation Techniques and Signal Processing MCQs
- 167. Information Theory and Communication MCqs
- 168. Two-Port Networks and Matching Techniques MCQs
- 169. Passive LC Filters MCQs
- 170. Transmission Line Fundamentals MCQs
- 171. RF Transmission Lines and Matching Techniques: MCQs
- 172. Tacheometry MCQS
- 173. Simple Stress and Strains MCQs
- 174. Laminar Flow MCQs
- 175. Construction equipments MCQs
- 176. Valuation MCQS
- 177. Urban Planning MCQs
- 178. Renewable Energy MCQs
- 179. Finance and Accounting MCQs
- 180. Indeterminate Structures-I MCQS
- 181. Tunnels MCQS

- 182. Advanced Waste-water treatment MCQS
- 183. Structural Engineering MCQs
- 184. Design of Slabs MCQS
- 185. Irrigation water requirement and Soil-Water-Crop relationship MCQS
- 186. Structural Joint MCQs
- 187. Cost effective construction techniques and equipments MCQs
- 188. Fluid Machines MCQs
- 189. Impact analysis MCQs
- 190. Basis of Structural Design and Connection Design MCQS
- 191. Hydrology MCQs
- 192. Design of R.C. Bridge MCQs
- 193. Seismic control of structures MCQs
- 194. Influence on Serviceability and Durability MCQs
- 195. Introduction of IC Engine MCQs
- 196. Systems With Two Degrees of Freedom MCQs
- 197. Governor Mechanisms MCQs
- 198. Emissions Norms & Measurement MCQs
- 199. SQC-Control charts MCQs
- 200. Refrigeration & Cooling MCQs